



Chapter-3

(Principle of Resonance in Series Circuit)

What is the resonance in series circuit?

Series resonance is a resonance condition that usually occurs in series circuits, where the current becomes a maximum for a particular voltage. In series resonance, the current is maximum at resonant frequency. The series resonance current curve increases to a maximum at resonance then decreases as resonance is passed.

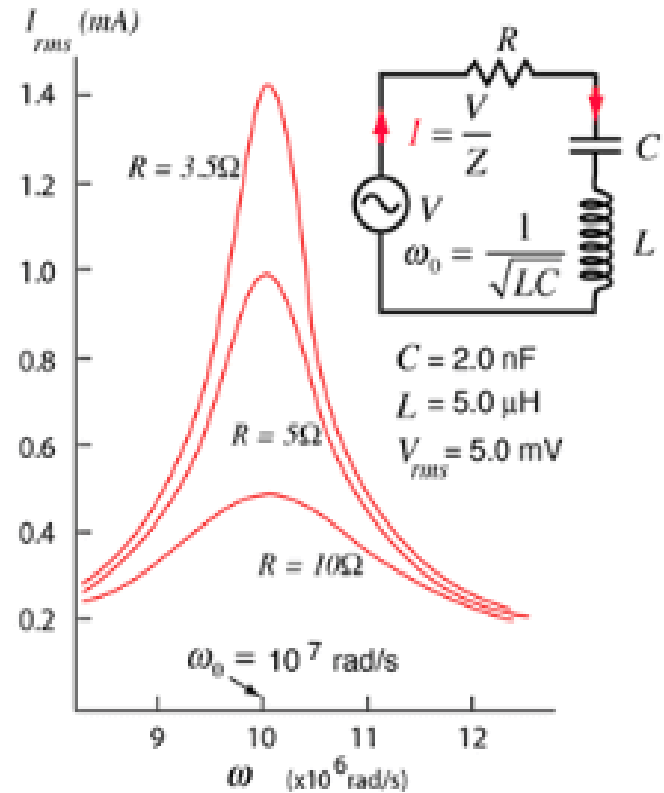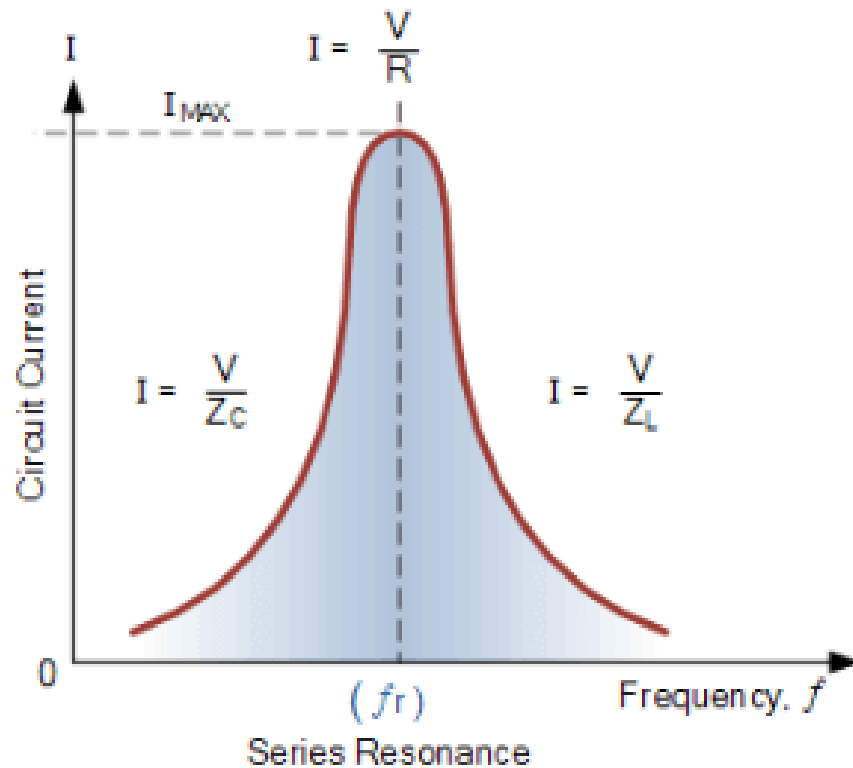
What is the Resonance in Series RLC Circuit?



Electrical 4 U

Series RLC Circuit

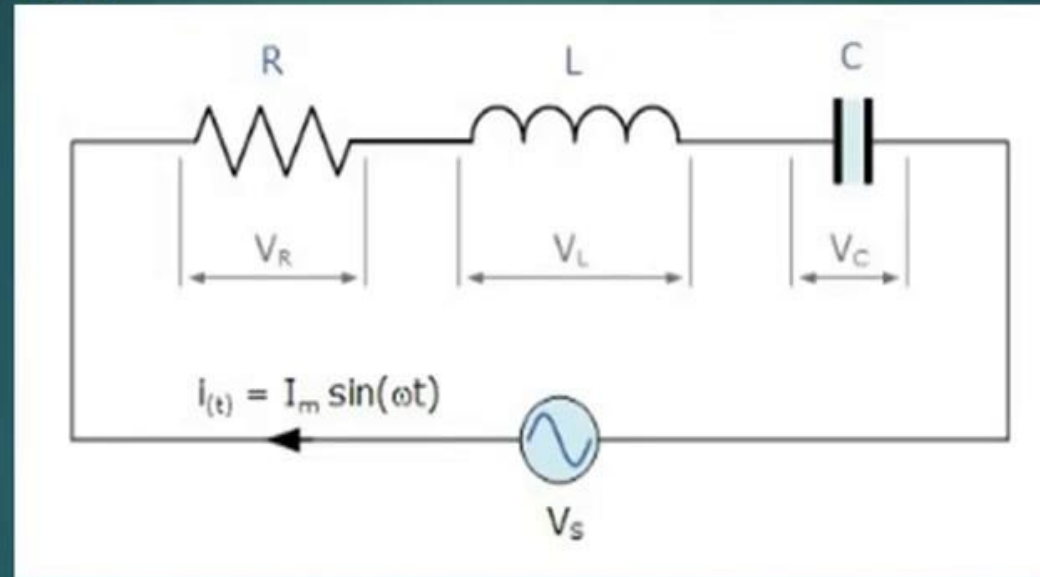- ▶ When resistor, inductor and capacitor are connected in series across a voltage supply, the circuit so obtained is called series RLC circuit.



- ▶ The three basic passive components: resistance (R), inductance (L), and capacitance (C) have very different phase relationships to each other when connected to a sinusoidal AC supply.

Series Resonance

Total impedance of series RLC Circuit is

$$Z_{\text{Total}} = R + jX_L - jX_C$$


$$Z_{\text{Total}} = R + j(X_L - X_C)$$

At resonance

$$X_L = X_C$$

The impedance now reduce to

$$Z_{\text{Total}} = R$$

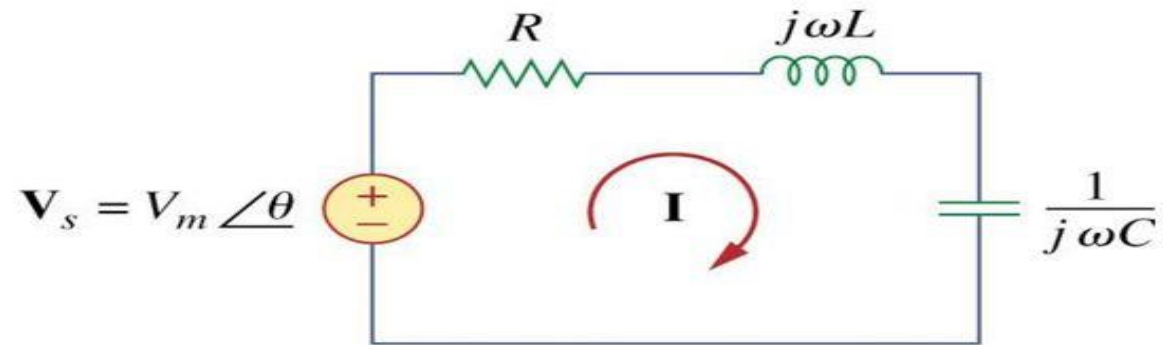

The current at resonance

$$I_m = \frac{V_s}{Z_{\text{Total}}} = \frac{V_m}{R}$$