





# Chapter-5

( Understand the Different types of special diodes)

Presented by

Hasan Murad Munna

# What is a Zener Diode?

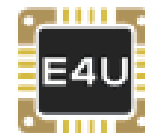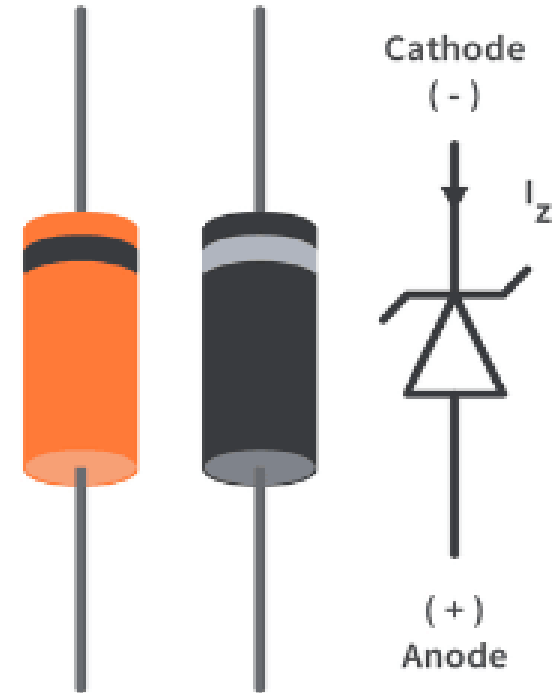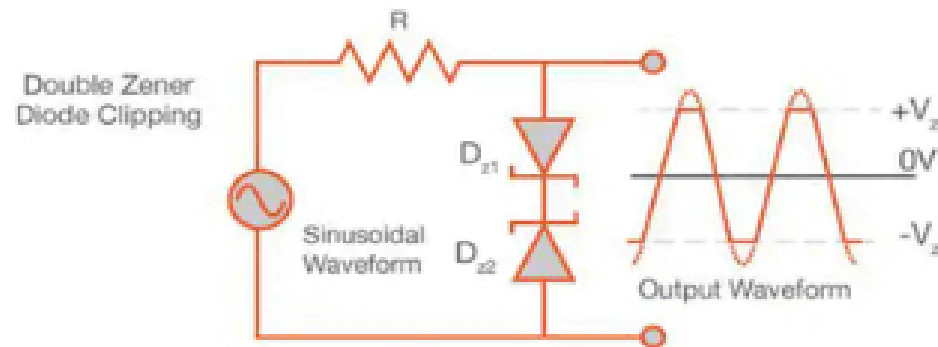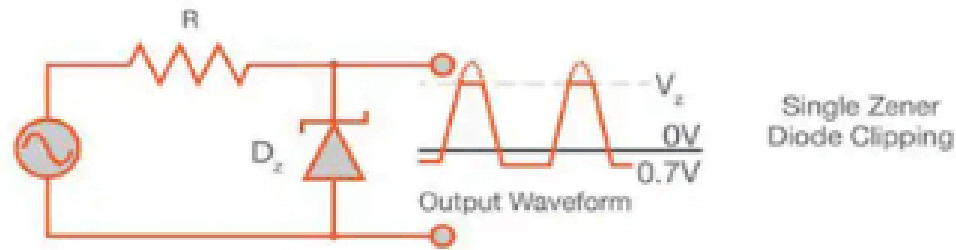

Electrical 4 U

# ZENER DIODE AS VOLTAGE REGULATOR

