


# Chapter:6

(Understand the effect of Bandwidth & Q-factor in parallel Resonance)

Lecture-1
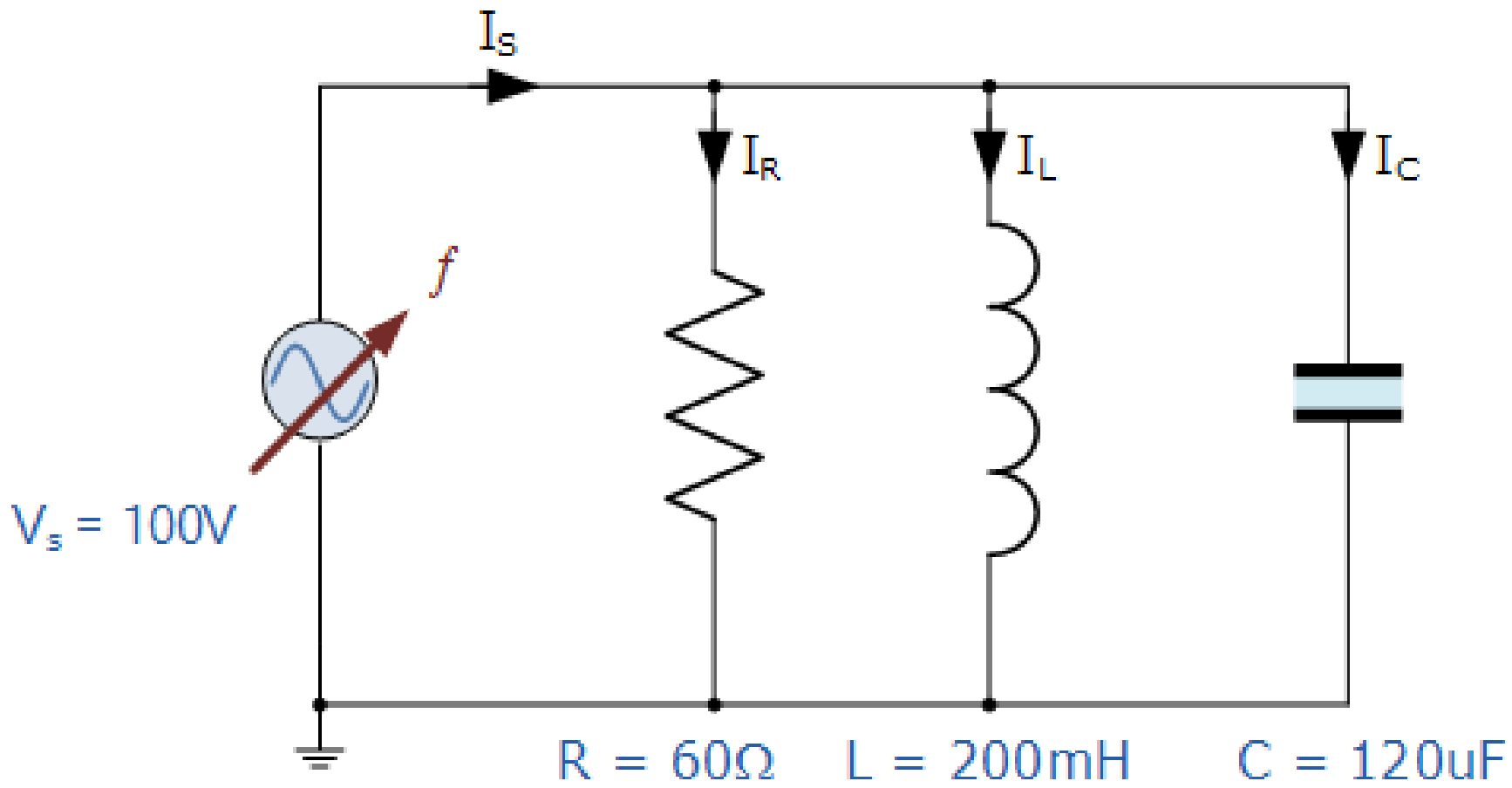
## Definition of the effect of Bandwidth & Q-factor in parallel Resonance

- Bandwidth:
- Bandwidth of a Parallel Resonance Circuit;
- The bandwidth of a parallel resonance circuit is defined in exactly the same way as for the series resonance circuit. The upper and lower cut-off frequencies given as: upper and lower respectively denote the half-power frequencies where the power dissipated in the circuit is half of the full power dissipated at the resonant frequency  $0.5(I^2 R)$  which gives us the same -3dB points at a current value that is equal to 70.7% of its maximum resonant value,  $(0.707 \times I)^2 R$



- Q-Factor:
- if the resonant frequency remains constant, an increase in the quality factor, Q will cause a decrease in the bandwidth and likewise, a decrease in the quality factor will cause an increase in the bandwidth as defined by:
- $BW = f_r / Q$  or  $BW = f_{upper} - f_{lower}$
- Also changing the ratio between the inductor, L and the capacitor, C, or the value of the resistance, R the bandwidth and therefore the frequency response of the circuit will be changed for a fixed resonant frequency. This technique is used extensively in tuning circuits for radio and television transmitters and receivers.
- The selectivity or Q-factor for a parallel resonance circuit is generally defined as the ratio of the circulating branch currents to the supply current and is given as:

- Q-factor for a parallel resonance circuit:
- Note that the Q-factor of a parallel resonance circuit is the inverse of the expression for the Q-factor of the series circuit. Also in series resonance circuits the Q-factor gives the voltage magnification of the circuit, whereas in a parallel circuit it gives the current magnification.

