

# Chapter:10

(Measurement of Single Phase Power)

Lecture-1

## Derive the equation ( $P=EI \cos \theta$ )

According to Joules law, the instantaneous power at any moment is the same as in a DC circuit.

$$P(t) = V(t) \cdot I(t)$$

Average power = Time average of the power over one period.

$$\text{i.e. } P_{\text{av}} = \frac{1}{T} \int_0^T P(t) dt$$

$$= \frac{1}{T} \int_0^T V(t) \cdot I(t) dt$$

For current driven circuit,

$$V(t) = V_{\text{max}} \sin(\omega t + \phi) = ZI_{\text{max}} \sin(\omega t + \phi)$$

$$\text{and } I(t) = I_{\text{max}} \sin(\omega t)$$

So,

$$P_{\text{av}} = \frac{1}{T} \int_0^T [ZI_{\text{max}} \sin(\omega t + \phi)] \cdot [I_{\text{max}} \sin(\omega t)] dt$$

$$= \frac{ZI_{\text{max}}^2}{T} \int_0^T \sin(\omega t + \phi) \cdot \sin(\omega t) dt$$

$$= \frac{ZI_{\text{max}}^2}{T} \int_0^T [\sin(\omega t) \cos\phi + \cos(\omega t) \sin\phi] \cdot \sin(\omega t) dt$$


$$= \frac{ZI_{\text{max}}^2}{T} \left[ \cos\phi \int_0^T \sin^2 \omega t dt + \sin\phi \int_0^T \sin(\omega t) \cos(\omega t) dt \right]$$

$$= \frac{ZI_{\text{max}}^2}{T} \left[ \cos(\phi) \times \frac{T}{2} + \sin\phi \times 0 \right]$$

$$= \frac{ZI_{\text{max}}^2}{2} \left[ \cos(\phi) \right]$$

## Circuit Diagram Connecting Wattmeter in a Single Phase Circuit:

- Wattmeter's are generally used to measure power in the circuits. A wattmeter principally consists of two coils, one coil is called the current coil, and the other the pressure or voltage coil. A diagrammatic representation of a wattmeter connected to measure power in a single phase circuit is shown in Fig. 9.42.

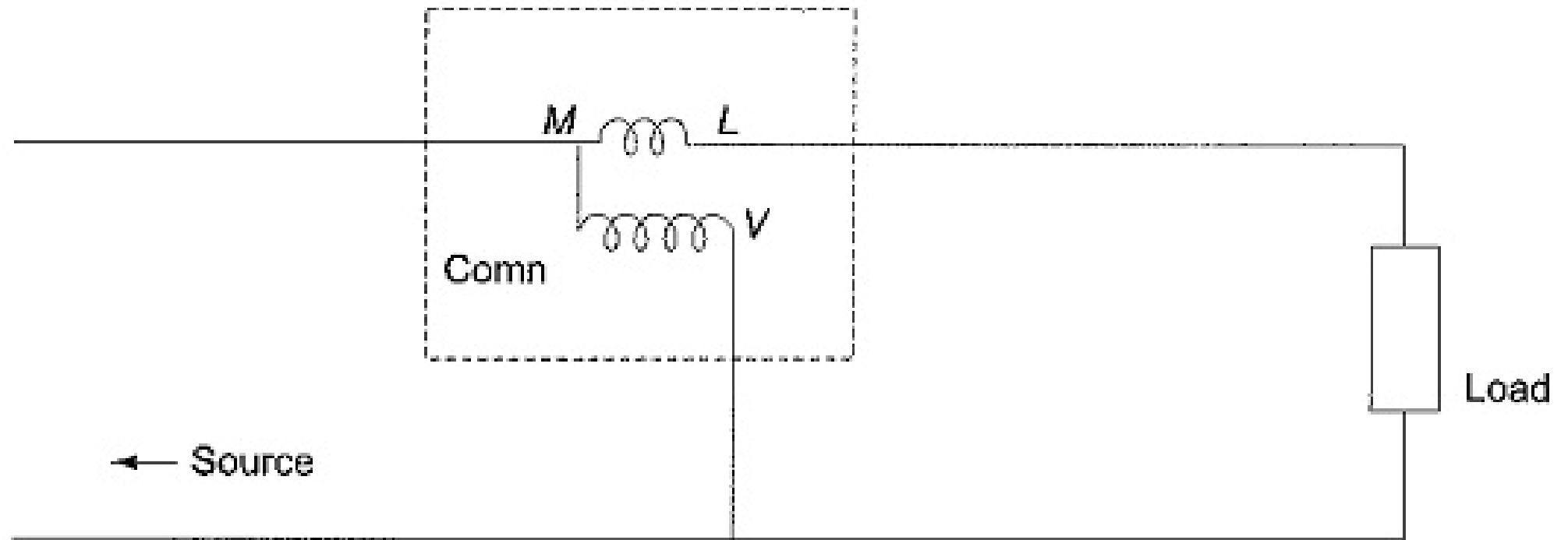

**Fig. 9.42**

- The coil represented with less number of turns between M and L is the current coil, which carries the current in the load and has very low impedance. The coil with more number of turns between the common terminal and V is the pressure coil, which is connected across the load and has high impedance.
- The load voltage is impressed across the pressure coil. The terminal M denotes the mains side, L denotes load side, common denotes the common point of current coil and pressure coil, and V denotes the second terminal of the pressure coil, usually selected as per the range of the load voltage in the circuit. From the figure, it is clear that a wattmeter has four terminals, two for current coil and two for potential coil. When the current flow through the two coils, they set up magnetic fields in space.