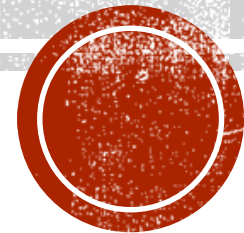


SEQUENTIAL LOGIC SYSTEM

Chapter 1 : Understand the features of Sequential Logic Circuits



Course Instructor

Afifa Hoque

DEFINITION OF SEQUENTIAL LOGIC CIRCUIT


○ Sequential logic consists of :


1. Memory elements :

- flip flops
- Store the **present** states

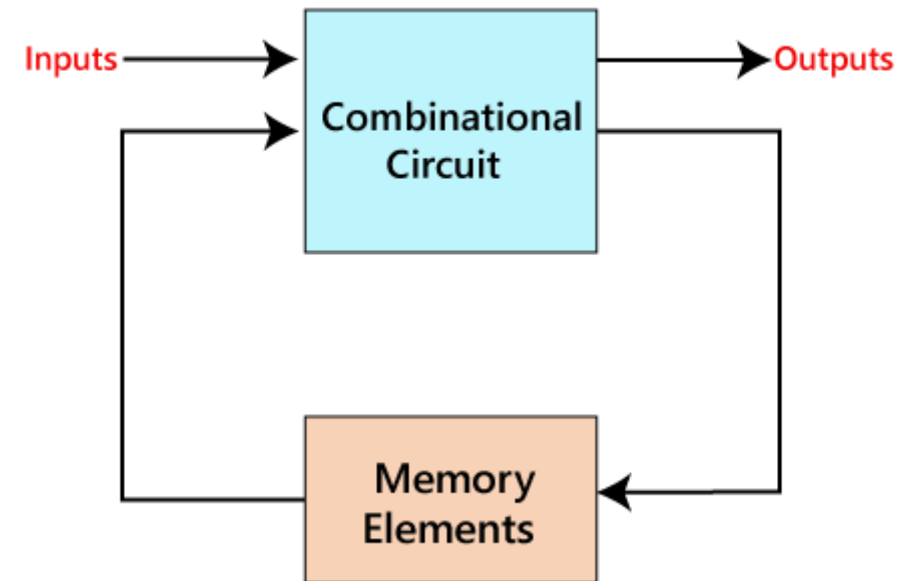2. Combinational Logic :

- Computes the **outputs** of the circuit
 - a. Outputs depend on Inputs and current state
- Computes the **next state** of the circuit
 - a. Next state also depends on the inputs and the present state



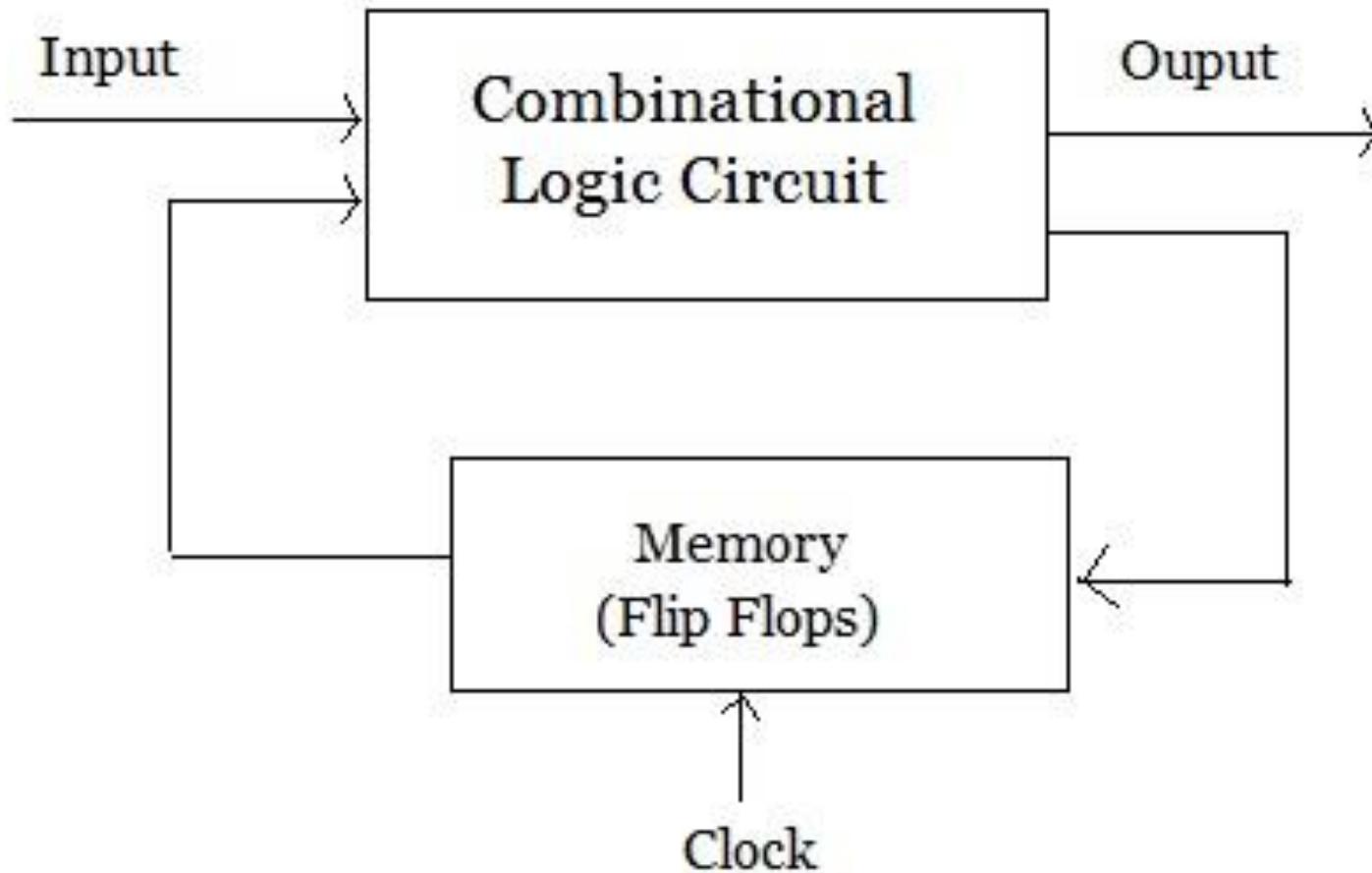


TYPES OF SEQUENTIAL CIRCUIT

1. Synchronous Sequential Logic Circuit :
 - Uses a clock signal as an additional input
 - Changes in the memory elements are controlled by the clock
 - Changes happen at discrete instances of time



(CONT.)

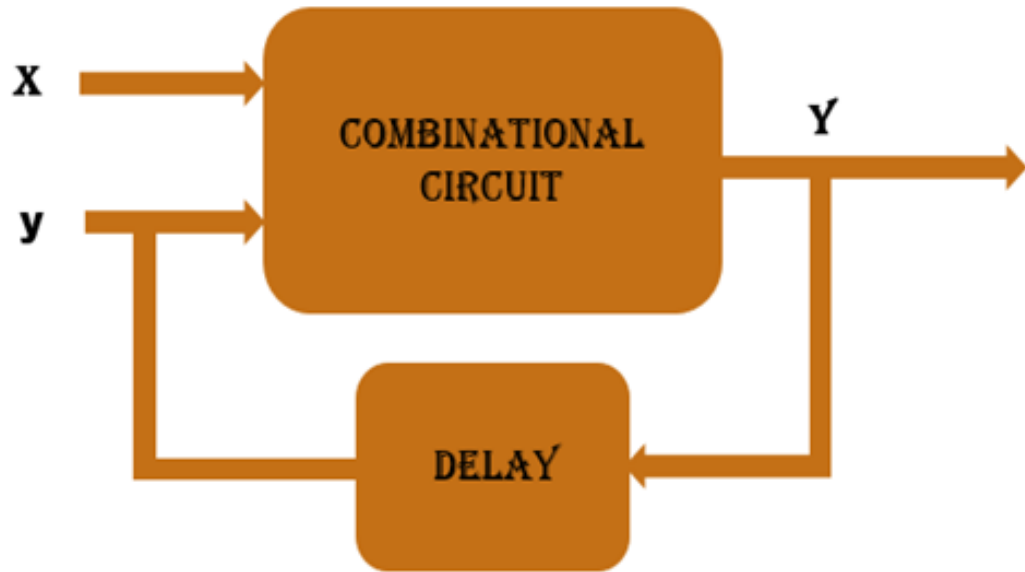


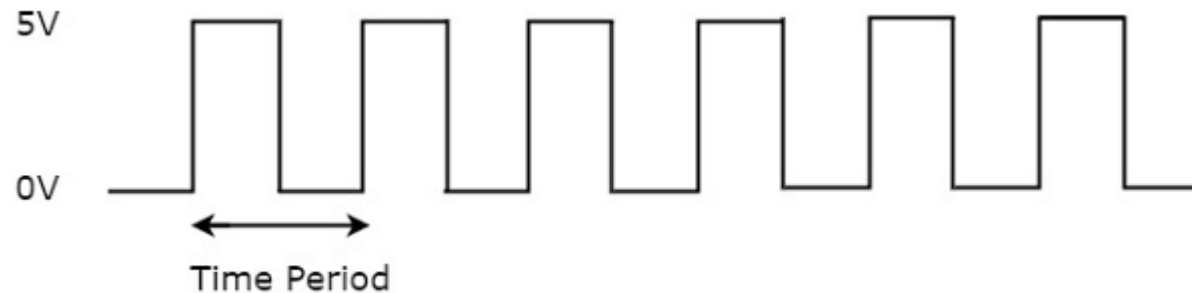1. **Asynchronous Sequential Circuit**
 - No clock signal
 - Changes in the memory elements can happen at any instance of time



DEFINITIONS

- Clock : A signal used to synchronize the operations of an electronic system.



- Timing Diagram: A timing diagram is a **graph of the output of a logic gate with respect to the inputs of the gate.**



(CONT.)

- Latch :

- **Basic storage elements that operate with signal levels**
- Controlled by a clock transition are flip-flops
- Level-sensitive devices
- Useful for the design of the asynchronous sequential circuit


- **Flip-Flop :**

- **An electronic circuit with two stable states that can be used to store binary data**
- Stored data can be changed by applying varying inputs
- **Five different types of flip flops are:**
 - 1) Set-Reset (SR) flip-flop or Latch.
 - 2) JK(**Jack Kilby**) flip-flop.
 - 3) D (Data or Delay) flip-flop.
 - 4) T (Toggle) flip-flop.
 - 5) MS-JK(Master Slave flip-flop



OPERATION OF SEQUENTIAL LOGIC SYSTEM

- Sequential logic is a type of logic circuit whose output depends not only on the present value of its input signals but **on the sequence of past inputs, the input history as well**. This is in contrast to combinational logic, whose output is a function of only the present input.
- Sequential circuits are essentially combinational circuits with feedback. A block diagram of a generalised sequential circuit is shown in Figure below. The generalised circuit contains a block of combinational logic which has two sets of inputs and two sets of outputs. The inputs are:

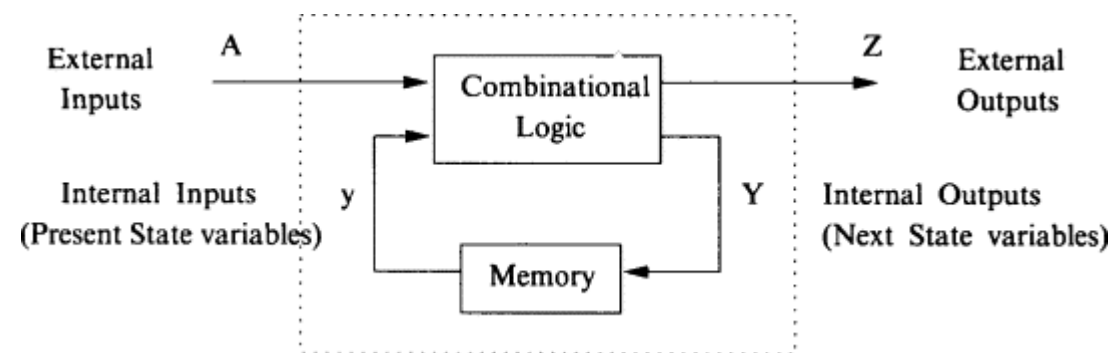

DIFFERENCE BETWEEN SYNCHRONOUS & ASYNCHRONOUS CIRCUIT

Synchronous Circuit

- Synchronous sequential circuits are digital circuits governed by clock signals.
- The synchronous sequential circuits are slower in its operation speed. This is due to the propagation delay of clock signal in reaching all elements of the circuit.
- The distributed clock signal consumes large power and dissipates large amount of heat.
- Synchronous circuits are used in counters, shift registers, memory unit.

Asynchronous Circuit

- Asynchronous sequential circuits are digital circuits that are not driven by clock. They can be called as self-timed circuits.
- The asynchronous sequential circuits are comparatively faster. Here, there is no clock signal but only the propagation delay of logic gates.
- Power consumption and heat dissipation are comparatively lower.
- Asynchronous circuits are used in low power and high speed operations.



THANK YOU

