

# Sequential Logic System

## Chapter Two

Prepared By  
Afifa Hoque  
Jr. Instructor  
DIIT, CTG.


# Understand Flip-Flop

- flip-flop or latch is a circuit that has two stable states and can be used to store state information – a bistable multivibrator. The circuit can be made to change state by signals applied to one or more control inputs and will have one or two outputs.


# Types of Flip Flop

- **There are basically four different types of flip flops and these are:**
- Set-Reset (SR) flip-flop or Latch.
- JK flip-flop.
- D (Data or Delay) flip-flop.
- T (Toggle) flip-flop.

# SR Flip Flop

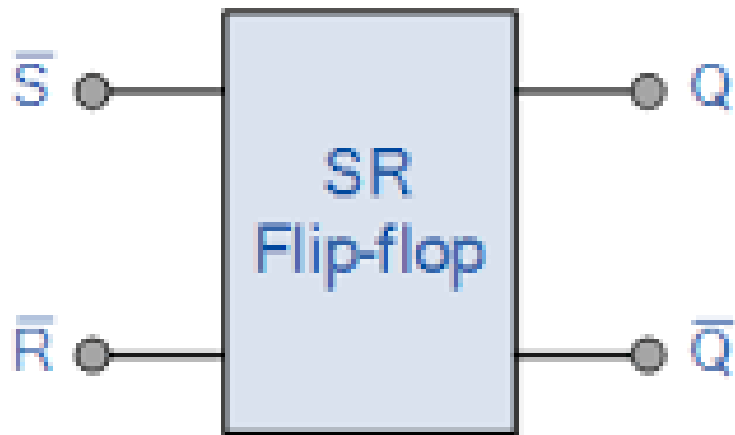

Symbol

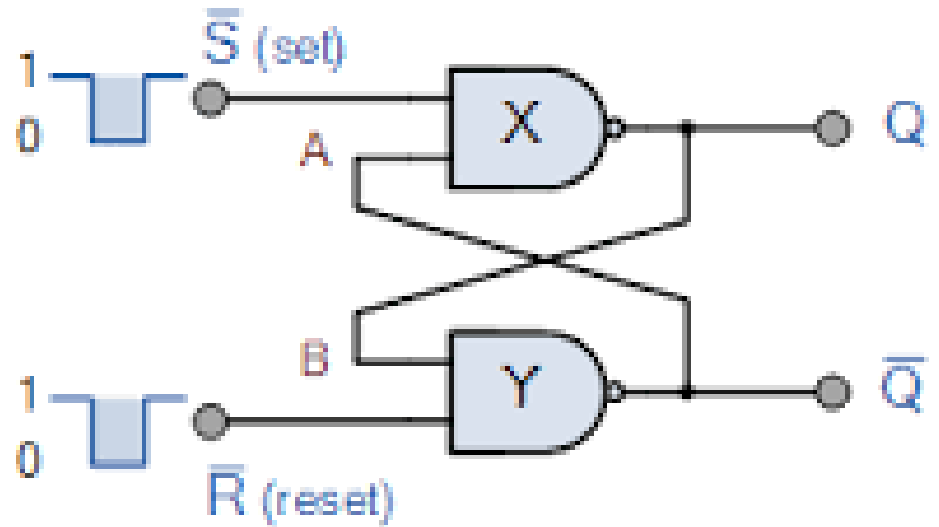

Circuit

- Truth Table


| S | R | Q | Q' |
|---|---|---|----|
| 1 | 0 | 1 | 0  |
| 0 | 0 | 1 | 0  |
| 0 | 1 | 0 | 1  |
| 0 | 0 | 0 | 1  |
| 1 | 1 | 0 | 0  |

After S = 1 and R = 0


After S = 0 and R = 1

Invalid

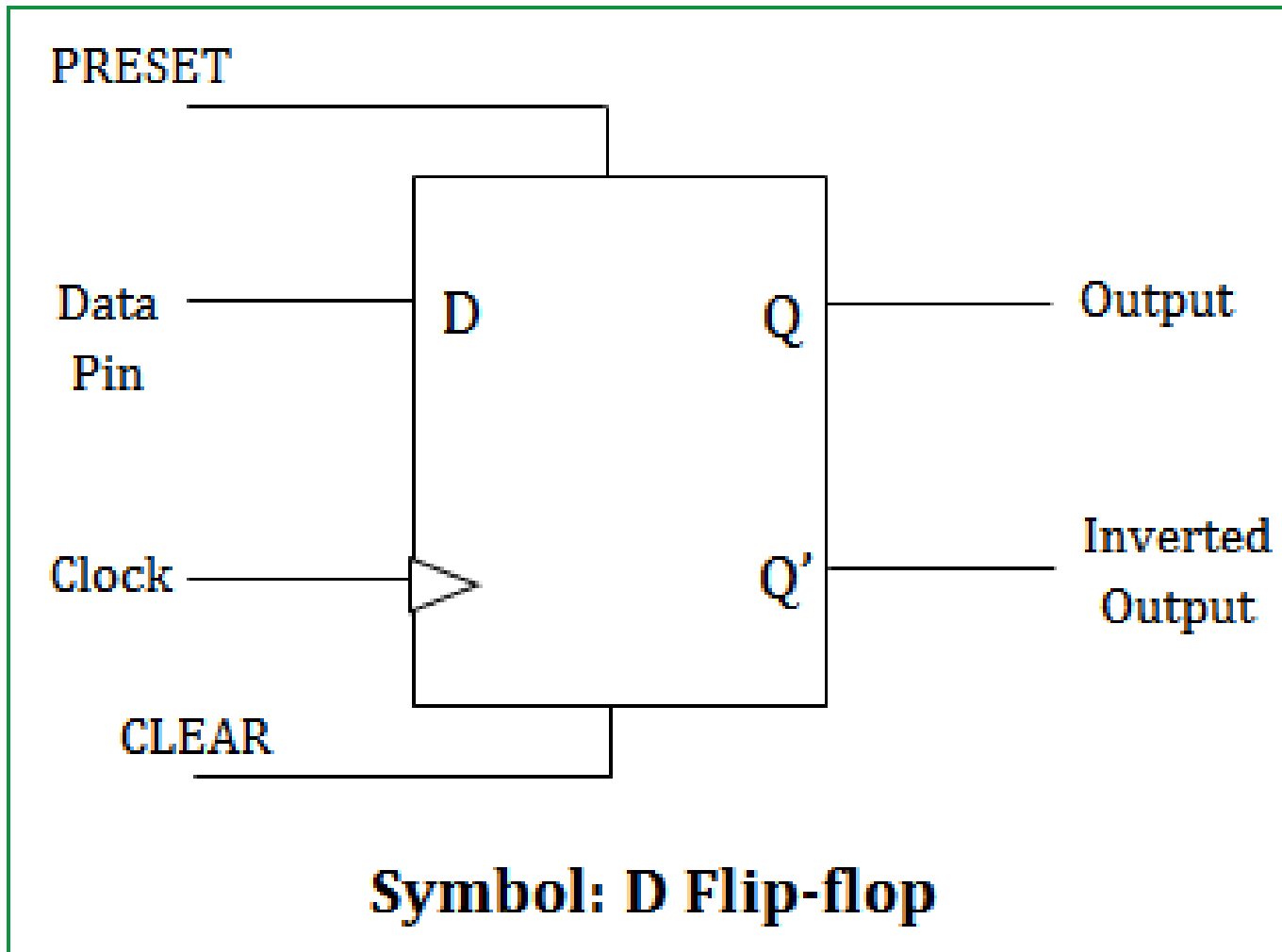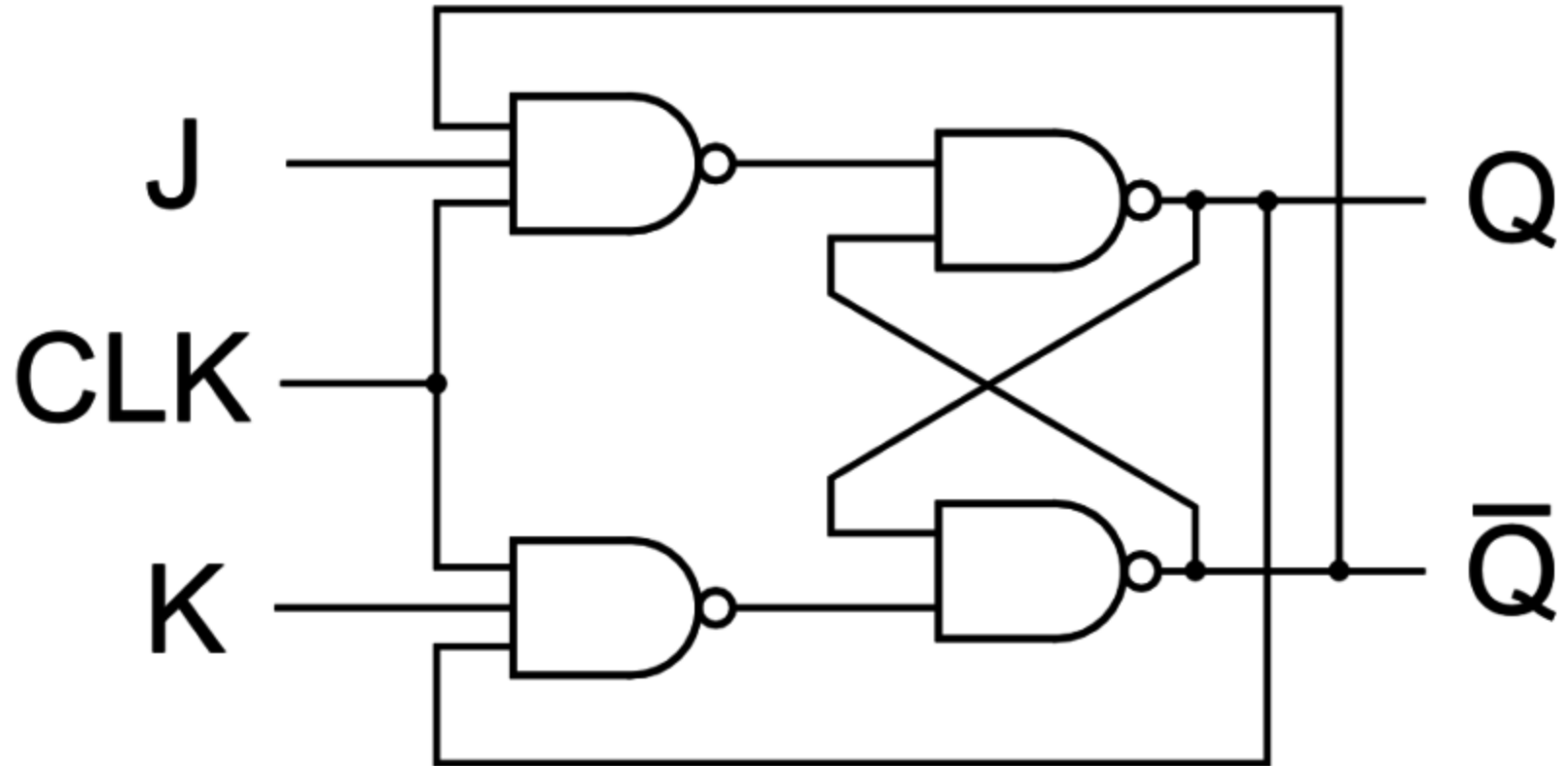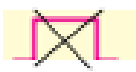
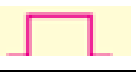

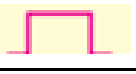
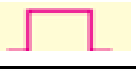
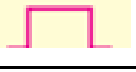

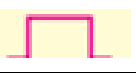

# D flip flop



# J-K Flip Flop




- J-K Flip Flop

| Trigger   | Inputs |   | Output        |    |            |    | Inference |
|---|--------|---|---------------|----|------------|----|-----------|
|   |        |   | Present State |    | Next State |    |           |
| CLK   | J      | K | Q             | Q' | Q          | Q' |           |
|    | x      | x | -             |    | -          |    | Latched   |
|    | 0      | 0 | 0             | 1  | 0          | 1  | No Change |
|    |        |   | 1             | 0  | 1          | 0  |           |
|    | 0      | 1 | 0             | 1  | 0          | 1  | Reset     |
|    |        |   | 1             | 0  | 0          | 1  |           |
|   | 1      | 0 | 0             | 1  | 1          | 0  | Set       |
|  |        |   | 1             | 0  | 1          | 0  |           |
|  | 1      | 1 | 0             | 1  | 1          | 0  | Toggles   |
|  |        |   | 1             | 0  | 0          | 1  |           |



# T flip flop

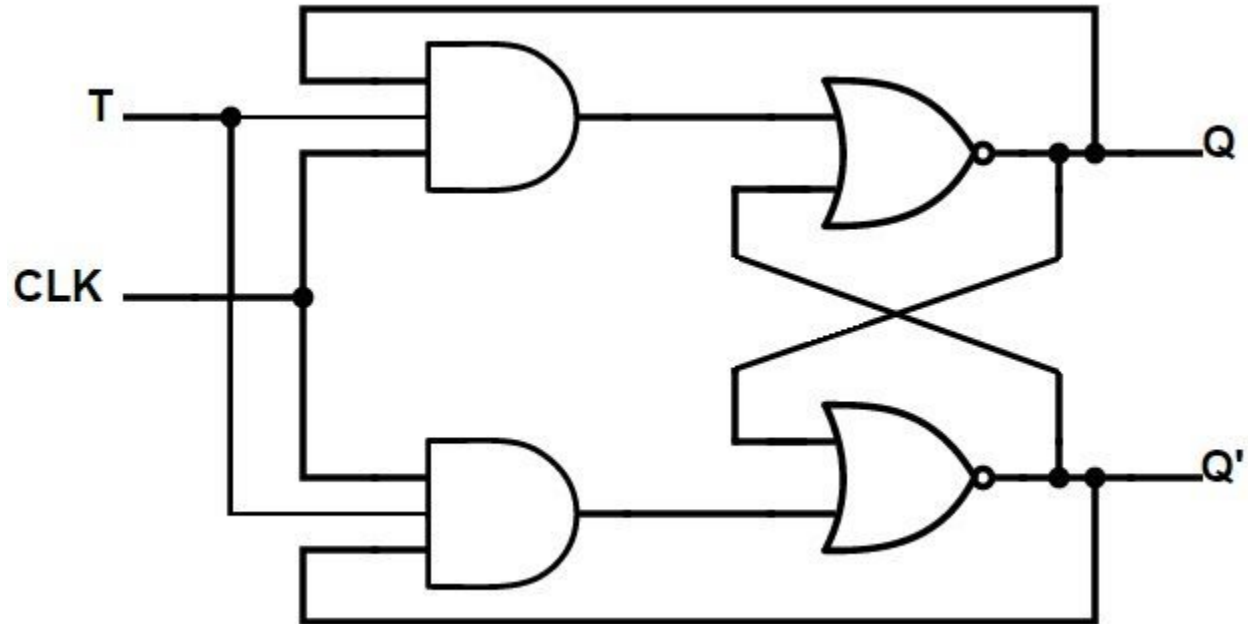

# Truth Table

| Input | Outputs       |            |
|-------|---------------|------------|
|       | Present State | Next State |
| T     | $Q_n$         | $Q_{n+1}$  |
| 0     | 0             | 0          |
| 0     | 1             | 1          |
| 1     | 0             | 1          |
| 1     | 1             | 0          |